 



→ Finite State Machines



trasformo il mio segnale  
di input asincrono in  
sincrono

# Finite-State-Machines

## Introduction

 

Sequential Digital Circuits can be:


- Synchronous → they use a clock signal (and edge-triggered FF)
- Asynchronous → they use asynchronous memory elements (latches)

Synchronous Digital Circuits are more robust because they are less sensitive to:

- Static and dynamic hazard (the system does not evolve towards unwanted states if clock signal period is longer than any switching time delay)
- Unwanted glitches and/or disturbs, affecting Actual State

# Finite-State-Machines

## Introduction

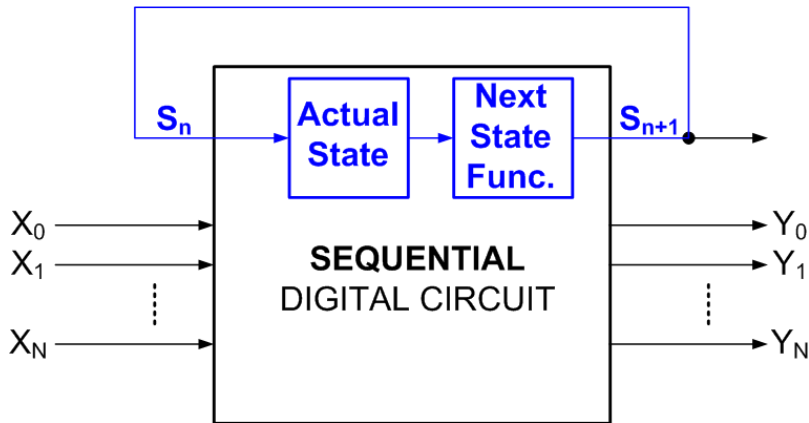

FSMs are COMPLETELY DEFINED BY the following signals:

- Input Signals ( $X$ )
- Output Signals ( $Y$ )

and

- States List (Actual State)
- Outputs Function ( $f_{OUT}$ )
- Next-State Function ( $f_{NS}$ )


# Finite-State-Machines

## Outline

- Introduction
- **Mealy and Moore FSM** ←←←
- State Diagram
- State Table
- Sequential Synchronous FSM Circuital Synthesis
- Exercise 1
- Exercise 2
- Exercise 3

# Finite-State-Machines

## Mealy FSMs

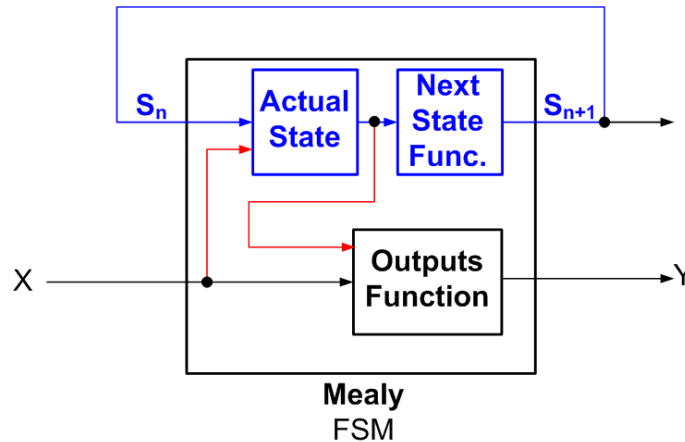


In Mealy-FSM the output  $Y$  is a function of both actual state ( $S_n$ ) and input ( $X$ ).

Mealy FSM are COMPLETELY DEFINED BY:

- Input Signals ( $X$ )
- Output Signals ( $Y$ )
- States List (Actual State)
- Outputs Function  $f_{OUT}$ , where  $Y = f_{OUT}(X, S_n)$
- Next-State Function  $f_{NS}$ , where  $S_{n+1} = f_{NS}(X, S_n)$

# Finite-State-Machines

## Moore FSMs

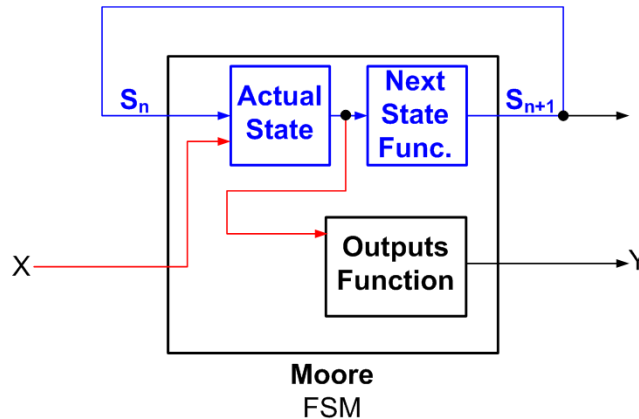


In Moore-FSM the output  $Y$  is a function of only actual state ( $S_n$ ).

Moore FSM are COMPLETELY DEFINED BY:

- Input Signals ( $X$ )
- Output Signals ( $Y$ )
- States List (Actual State)
- Outputs Function  $f_{OUT}$ , where  $Y = f_{OUT}(S_n)$
- Next-State Function  $f_{NS}$ , where  $S_{n+1} = f_{NS}(X, S_n)$

# Finite-State-Machines

## Mealy FSMs

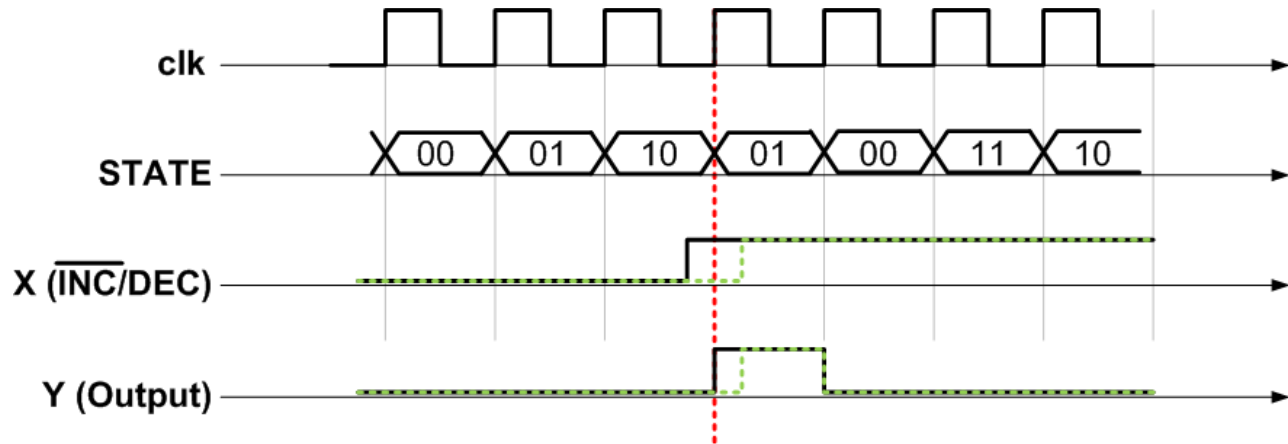

### Case Study → 2b-Counter with '01' Output Flag

Operation: Y (Output) is '1' when Counter State is "01" and X='1'

Input Signals: clk, X (increment or decrement signal)

Output Signals: STATE<0:1>, Y

Output Logic Function:  $Y = f_{OUT}(S_n, X) = \overline{S_n(1)} \cdot S_n(0) \cdot X$

→→→ **Mealy FSMs** can have asynchronous behavior (Y depends on X)

Time evolution depends on X delays

# Finite-State-Machines

## Design Procedure

### FSM Design Procedure

- **Define**

- o Input Signals (X)
- o Output Signals (Y)
- o States List (Actual State)

- **State-Diagram**

- o Graphical Representation of all states and transitions (from one state to another)

- **State-Table**

- o A table with two main columns regions:
  - The first region points the actual state ( $S_n$ ) and the input signals (X)
  - The second the next states and the output signals ( $S_{n+1}$  and Y)

- **Next-State Function  $f_{NS}$**

- o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

- **Outputs Function  $f_{OUT}$**

- o where  $Y = f_{OUT}(S_n)$  or  $Y = f_{OUT}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis




# Finite-State-Machines

## Outline

- Introduction
- Mealy and Moore FSM
- **State Diagram** ←←←
- State Table
- Sequential Synchronous FSM Circuital Synthesis
- Exercise 1
- Exercise 2
- Exercise 3

# Finite-State-Machines

## State-Diagram

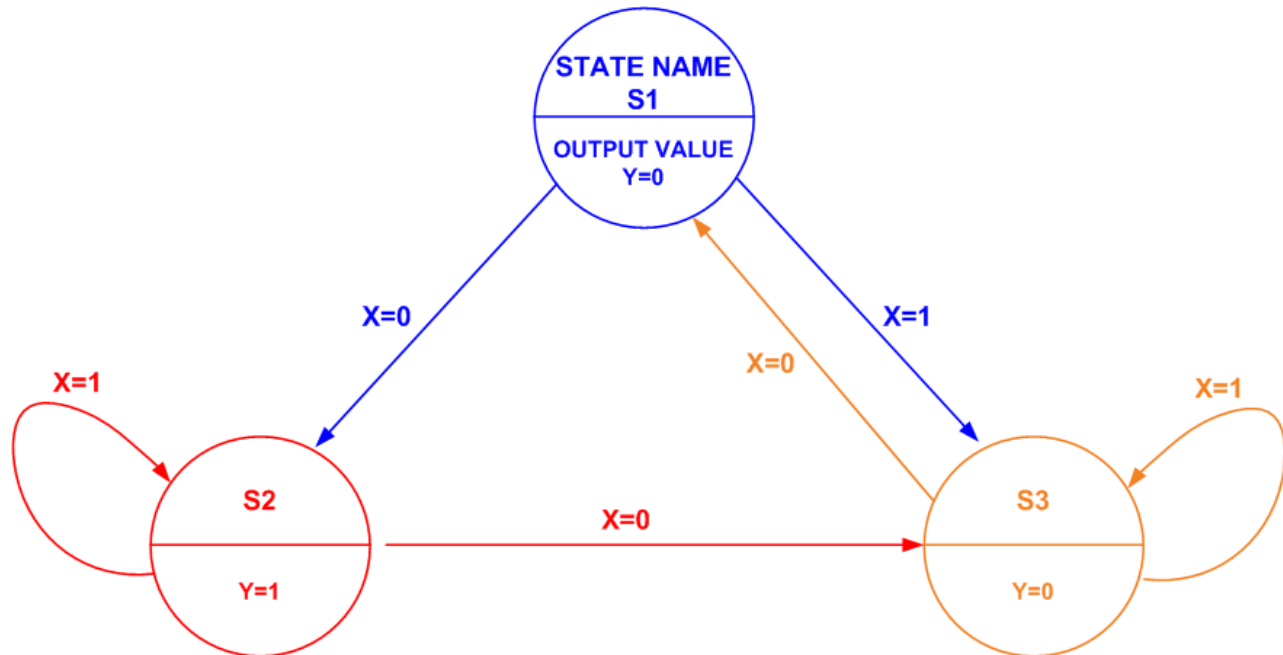

Each STATE has:

- State Name (Ex: S0, S1, S2, ..)
- Output Value (Ex: Y=0 or Y=1)
- Transition Arrows (one for each input value)


# Finite-State-Machines

## Outline

- Introduction
- Mealy and Moore FSM
- State Diagram
- **State Table** ←←←
- Sequential Synchronous FSM Circuital Synthesis
- Exercise 1
- Exercise 2
- Exercise 3

# Finite-State-Machines

## State-Table

 

ACTUAL STATE	INPUT	NEXT STATE	OUTPUT
S1	0	S2	Y=1
S1	1	S3	Y=0
S2	0	S3	Y=0
S2	1	S2	Y=1
S3	0	S1	Y=0
S3	1	S3	Y=0


**State Table**

Each STATE Table has the following columns:

- Actual State Name (Ex: S0, S1, S2, ..)
- Input Value (Ex: X=0 or X=1)
- Next State (Ex: S0, S1, S2, ..)
- Output Value (Ex: Y=0 or Y=1)

# Finite-State-Machines

## State-Table

 


ACTUAL STATE			INPUT	NEXT STATE			OUTPUT
S1	0	0	0	S2	0	1	Y=1
S1	0	0	1	S3	1	0	Y=0
S2	0	1	0	S3	1	0	Y=0
S2	0	1	1	S2	0	1	Y=1
S3	1	0	0	S1	0	0	Y=0
S3	1	0	1	S3	1	0	Y=0

Each STATE Table has the following columns:

- Actual State Name (Ex: S0, S1, S2, ..)
  - o **Each State has a specific binary code (EX: S1=00, S2=01, S3=10, etc)**
- Input Value (Ex: X=0 or X=1)
- Next State (Ex: S0, S1, S2, ..)
- Output Value (Ex: Y=0 or Y=1)

# Finite-State-Machines

## State-Table

 


ACTUAL STATE			INPUT	NEXT STATE			OUTPUT
S1	0	0	0	S2	0	1	Y=1
S1	0	0	1	S3	1	1	Y=0
S2	0	1	0	S3	1	1	Y=0
S2	0	1	1	S2	0	1	Y=1
S3	1	1	0	S1	0	0	Y=0
S3	1	1	1	S3	1	1	Y=0

Each STATE Table has the following columns:

- Actual State Name (Ex: S0, S1, S2, ..)
  - o Each State has a specific binary code (EX: S1=00, S2=01, S3=10, etc)
  - o In case of  $\leq 4$  states, Grey Code does not resolve unwanted states evolution (due to delay)
- Input Value (Ex: X=0 or X=1)
- Next State (Ex: S0, S1, S2, ..)
- Output Value (Ex: Y=0 or Y=1)

# Finite-State-Machines
 
## State-Table – Unwanted States and Transitions in Moore FSMs




ACTUAL STATE			NEXT STATE			OUTPUT
	S<1>	S<0>		S<1>	S<0>	
S2	1	0	S1	0	1	Y=0
S1	0	1	SX	x	x	Y=0
S3	1	1	S0	0	0	Y=1

- Let analyze the S2→S1 transition (look at the States Table)
- Contemporary switching is “statistically rare”
- Suppose S1 switches-down later than S0 switching-up
- The system is for a small time in S3=11 state
- In this state the output Y is 1, instead of 0

# Finite-State-Machines
 
## State-Table – Unwanted States and Transitions in Moore FSMs




### ☺ Good Points:

- State S3(=11) is only for a small time, since Moore-FSM are based on DFF that guarantees to evolve from S2 towards S1 state
- The system is naturally forced to evolve towards S1

### ☹ Bad Points

- Output Signal is '1' for a small time

 




# Finite-State-Machines

## Outline

- Introduction
- Mealy and Moore FSM
- State Diagram
- State Table
- **Sequential Synchronous FSM Circuitual Synthesis** ←←←
- Exercise 1
- Exercise 2
- Exercise 3

# Finite-State-Machines

## Moore-FSM Design

 

ACTUAL STATE S <sub>n</sub>			INPUT	NEXT STATE S <sub>n+1</sub>			OUTPUT
	Sn(1)	Sn(0)	X		Sn+1(1)	Sn+1(0)	Y
S1	0	0	0	S2	0	1	1
S1	0	0	1	S3	1	1	0
S2	0	1	0	S3	1	1	0
S2	0	1	1	S2	0	1	1
S3	1	1	0	S1	0	0	0
S3	1	1	1	S3	1	1	0

NEXT-STATE Function  $f_{NS}(S_n, X)$ :

- NEXT-STATE BITS ( $S_{n+1}(1)$  and  $S_{n+1}(0)$ ) are logic functions of
  - o  $S_n(1)$ ,  $S_n(0)$  (ACTUAL-STATE-BITS) and  $X$  (INPUT)
  - o Example:

- $S_{n+1}$  Logic Function

$$S_{n+1}(1) = f_{SN1}(S_n, X) = S_n(1) \cdot X + \overline{S_n(0)} \cdot X + \overline{S_n(1)} \cdot S_n(0) \cdot \overline{X}$$

$$S_{n+1}(0) = f_{SN0}(S_n, X) = \overline{S_n(1)} + X$$

- $Y$  Logic Function

$$Y = f_{OUT}(S_n) = \overline{S_n(0)} \cdot \overline{X} + \overline{S_n(1)} \cdot S_n(0) \cdot X$$

# Finite-State-Machines

## Outline

- Introduction
- Mealy and Moore FSM
- State Diagram
- State Table
- **Sequential Synchronous FSM Circuitual Synthesis**
- **Exercise 1** ←←←
- **Exercise 2** ←←←
- **Exercise 3** ←←←

# Finite-State-Machines

## Exercise

### Exercise 1:

Design a logic circuit able to detect two equal consecutive bits. In case of positive event, the Y output signal is 1, otherwise is 0. The circuit receives one single bit (X) and uses one single clock. Implement by Moore-FSM.

### Exercise 2:

Design a logic circuit that detects the 010 sequence. The circuit has only one digital input of 1 bit resolution.

### Exercise 3:

Design a logic circuit that detects the 110 sequence. The circuit has only one digital input of 1 bit resolution.

# Finite-State-Machines

## Exercise

### Exercise 1: ←←←

Design a logic circuit able to detect that two consecutive bits are equal. In case of positive event, the Y output signal is 1, otherwise is 0. The circuit receives one single bit (X) and uses one single clock. Implement by Moore-FSM.

#### FSM Design Procedure

- **Define**
  - o Input Signals (X)
  - o Output Signals (Y)
  - o States List (Actual State)
- **State-Diagram**
  - o Graphical Representation of all states and transitions (from one state to another)
- **State-Table**
  - o A table with two main columns regions:
    - The first region points the actual state ( $S_n$ ) and the input signals (X)
    - The second the next states and the output signals ( $S_{n+1}$  and Y)
- **Next-State Function  $f_{NS}$** 
  - o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis
- **Outputs Function  $f_{OUT}$** 
  - o where  $Y = f_{OUT}(S_n)$  or  $Y = f_{OUT}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

# Finite-State-Machines

## Exercise

### Exercise 1:

FSM Design Procedure

- **Define**
  - o Input Signals (X)
  - o Output Signals (Y)

*X, 1b resolution*

*Y, 1b resolution*

- **State-Diagram**
  - o Graphical Representation of all states and transitions (from one state to another)
- **State-Table**
  - o A table with two main columns regions:
    - The first region points the actual state ( $S_n$ ) and the input signals (X)
    - The second the next states and the output signals ( $S_{n+1}$  and Y)
- **Next-State Function  $f_{NS}$** 
  - o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis
- **Outputs Function  $f_{OUT}$** 
  - o where  $Y = f_{OUT}(S_n)$  or  $Y = f_{OUT}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

# Finite-State-Machines


## Exercise

### Exercise 1:

FSM Design Procedure

- **State-Diagram**

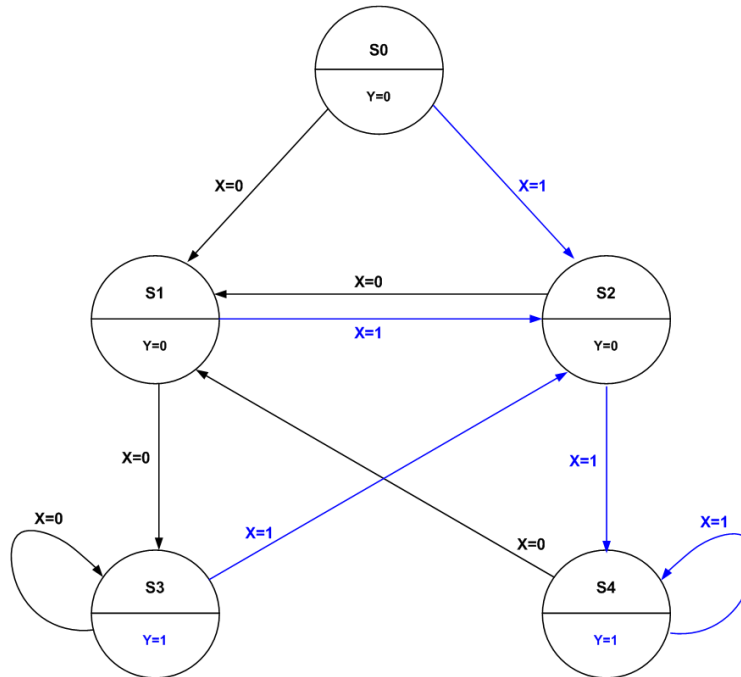- o Graphical Representation of all states and transitions (from one state to another)
- o Define States List → 5 STATES



# Finite-State-Machines

## Exercise

### Exercise 1:

#### FSM Design Procedure

##### ▪ State-Table

o A table with two main columns regions:

- The first region points the actual state ( $S_n$ ) and the input signals (X)
- The second the next states and the output signals ( $S_{n+1}$  and Y)

ACTUAL STATES				INPUT	NEXT STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	X	STATE NAME	$S_{n+1}(2)$	$S_{n+1}(1)$	$S_{n+1}(0)$	Y
S0	0	0	0	0	S1	0	0	1	0
S0	0	0	0	1	S2	0	1	0	0
S1	0	0	1	0	S3	0	1	1	1
S1	0	0	1	1	S2	0	1	0	0
S2	0	1	0	0	S1	0	0	1	0
S2	0	1	0	1	S4	1	0	0	1
S3	0	1	1	0	S3	0	1	1	1
S3	0	1	1	1	S2	0	1	0	0
S4	1	0	0	0	S1	0	0	1	0
S4	1	0	0	1	S4	1	0	0	1



# Finite-State-Machines

## Exercise

### Exercise 1:

FSM Design Procedure

- **Next-State Function  $f_{NS}$**

- o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

ACTUAL STATES				INPUT	NEXT STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	X	STATE NAME	$S_{n+1}(2)$	$S_{n+1}(1)$	$S_{n+1}(0)$	Y
S0	0	0	0	0	S1	0	0	1	0
S0	0	0	0	1	S2	0	1	0	0
S1	0	0	1	0	S3	0	1	1	1
S1	0	0	1	1	S2	0	1	0	0
S2	0	1	0	0	S1	0	0	1	0
S2	0	1	0	1	S4	1	0	0	1
S3	0	1	1	0	S3	0	1	1	1
S3	0	1	1	1	S2	0	1	0	0
S4	1	0	0	0	S1	0	0	1	0
S4	1	0	0	1	S4	1	0	0	1

Critical Transitions occur when at least two  $S_n$  bits contemporarily change

# Finite-State-Machines

## Exercise

### Exercise 1:


FSM Design Procedure

- **Next-State Function  $f_{NS}$**

- o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

ACTUAL STATES				INPUT	NEXT STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	X	STATE NAME	$S_{n+1}(2)$	$S_{n+1}(1)$	$S_{n+1}(0)$	Y
S2	0	1	0	0	S1	0	0	1	0

 Critical Transitions occur when two  $S_n$  bits contemporarily change:  $010 \rightarrow 001$



non riesco a cambiare  
due bit contemporaneamente

mi va bene perché  
 $Y=0$

# Finite-State-Machines

## Exercise

### Exercise 1:


FSM Design Procedure

- **Next-State Function  $f_{NS}$**

- o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

ACTUAL STATES				INPUT	NEXT STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	X	STATE NAME	$S_{n+1}(2)$	$S_{n+1}(1)$	$S_{n+1}(0)$	Y
S2	0	1	0	1	S4	1	0	0	1

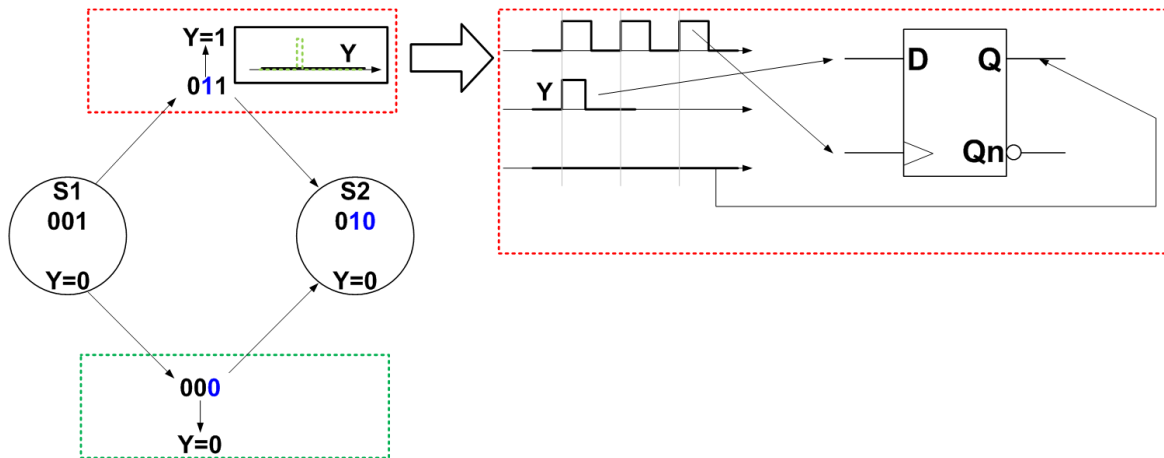Critical Transitions occur when two  $S_n$  bits contemporarily change: 001  $\rightarrow$  010



# Finite-State-Machines

## Exercise

### Exercise 1:


FSM Design Procedure

- **Next-State Function  $f_{NS}$**

- o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

ACTUAL STATES				INPUT	NEXT STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	X	STATE NAME	$S_{n+1}(2)$	$S_{n+1}(1)$	$S_{n+1}(0)$	Y
S2	0	1	0	1	S4	1	0	0	1

 Critical Transitions occur when two  $S_n$  bits contemporarily change:  $010 \rightarrow 100$



# Finite-State-Machines

## Exercise

### Exercise 1:


FSM Design Procedure

- **Next-State Function  $f_{NS}$**

- o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

ACTUAL STATES				INPUT	NEXT STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	X	STATE NAME	$S_{n+1}(2)$	$S_{n+1}(1)$	$S_{n+1}(0)$	Y
S4	1	0	0	0	S1	0	0	1	0

 Critical Transitions occur when two  $S_n$  bits contemporarily change:  $100 \rightarrow 001$



# Finite-State-Machines

## Exercise

### Exercise 1:

FSM Design Procedure

- **Next-State Function  $f_{NS}$**

- o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

ACTUAL STATES				INPUT	NEXT STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	X	STATE NAME	$S_{n+1}(2)$	$S_{n+1}(1)$	$S_{n+1}(0)$	Y
S0	0	0	0	0	S1	0	0	1	0
S0	0	0	0	1	S2	0	1	0	0
S1	0	0	1	0	S3	0	1	1	1
S1	0	0	1	1	S2	0	1	0	0
S2	0	1	0	0	S1	0	0	1	0
S2	0	1	0	1	S4	1	0	0	1
S3	0	1	1	0	S3	0	1	1	1
S3	0	1	1	1	S2	0	1	0	0
S4	1	0	0	0	S1	0	0	1	0
S4	1	0	0	1	S4	1	0	0	1

$S_{n+1}(2)$		$S_n(2) S_n(1)$			
		00	01	11	10
$S_n(0) X$	00	0	0	x	0
	01	0	1	x	1
	11	0	0	x	x
	10	0	0	x	x

$$S_{n+1}(2) = S_n(1) \cdot \overline{S_n(0)} \cdot X + S_n(2) \cdot X$$

# Finite-State-Machines

## Exercise

### Exercise 1:

FSM Design Procedure

- **Next-State Function  $f_{NS}$**

- o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

ACTUAL STATES				INPUT	NEXT STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	X	STATE NAME	$S_{n+1}(2)$	$S_{n+1}(1)$	$S_{n+1}(0)$	Y
S0	0	0	0	0	S1	0	0	1	0
S0	0	0	0	1	S2	0	1	0	0
S1	0	0	1	0	S3	0	1	1	1
S1	0	0	1	1	S2	0	1	0	0
S2	0	1	0	0	S1	0	0	1	0
S2	0	1	0	1	S4	1	0	0	1
S3	0	1	1	0	S3	0	1	1	1
S3	0	1	1	1	S2	0	1	0	0
S4	1	0	0	0	S1	0	0	1	0
S4	1	0	0	1	S4	1	0	0	1

$S_{n+1}(1)$		$S_n(2) S_n(1)$			
		00	01	11	10
$S_n(0) X$	00	0	0	x	0
	01	1	0	x	0
	11	1	1	x	x
	10	1	1	x	x

$$S_{n+1}(1) = S_n(0) + \overline{S_n(2)} \cdot \overline{S_n(1)} \cdot X$$

# Finite-State-Machines

## Exercise

### Exercise 1:

FSM Design Procedure

- **Next-State Function  $f_{NS}$**

- o where  $S_{n+1} = f_{NS}(X, S_n)$  by KMAPs or COMBINATORY logic synthesis

ACTUAL STATES				INPUT	NEXT STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	X	STATE NAME	$S_{n+1}(2)$	$S_{n+1}(1)$	$S_{n+1}(0)$	Y
S0	0	0	0	0	S1	0	0	1	0
S0	0	0	0	1	S2	0	1	0	0
S1	0	0	1	0	S3	0	1	1	1
S1	0	0	1	1	S2	0	1	0	0
S2	0	1	0	0	S1	0	0	1	0
S2	0	1	0	1	S4	1	0	0	1
S3	0	1	1	0	S3	0	1	1	1
S3	0	1	1	1	S2	0	1	0	0
S4	1	0	0	0	S1	0	0	1	0
S4	1	0	0	1	S4	1	0	0	1

		$S_{n+1}(0)$			
		$S_n(2)$	$S_n(1)$	$S_n(0)$	X
$S_n(0)$	00	1	1	x	1
	01	0	0	x	0
	11	0	0	x	x
	10	1	1	x	x

$$S_{n+1}(0) = \bar{X}$$



# Finite-State-Machines

## Exercise

### Exercise 1:

FSM Design Procedure

- **Outputs Function  $f_{OUT}$** 
  - o where  $Y=f_{OUT}(S_n)$  by KMAPs or COMBINATORY logic synthesis

STATES				OUTPUT
STATE NAME	$S_n(2)$	$S_n(1)$	$S_n(0)$	Y
S0	0	0	0	0
S1	0	0	1	0
S2	0	1	0	0
S3	0	1	1	1
S4	1	0	0	1
SX	1	0	1	X
SX	1	1	0	X
SX	1	1	1	X


Y		Sn(2) Sn(1)			
		00	01	11	10
Sn(0)	0	0	0	x	1
	1	0	1	x	x

$$Y = S_n(2) + S_n(1) \cdot S_n(0)$$

# Finite-State-Machines

## Exercise
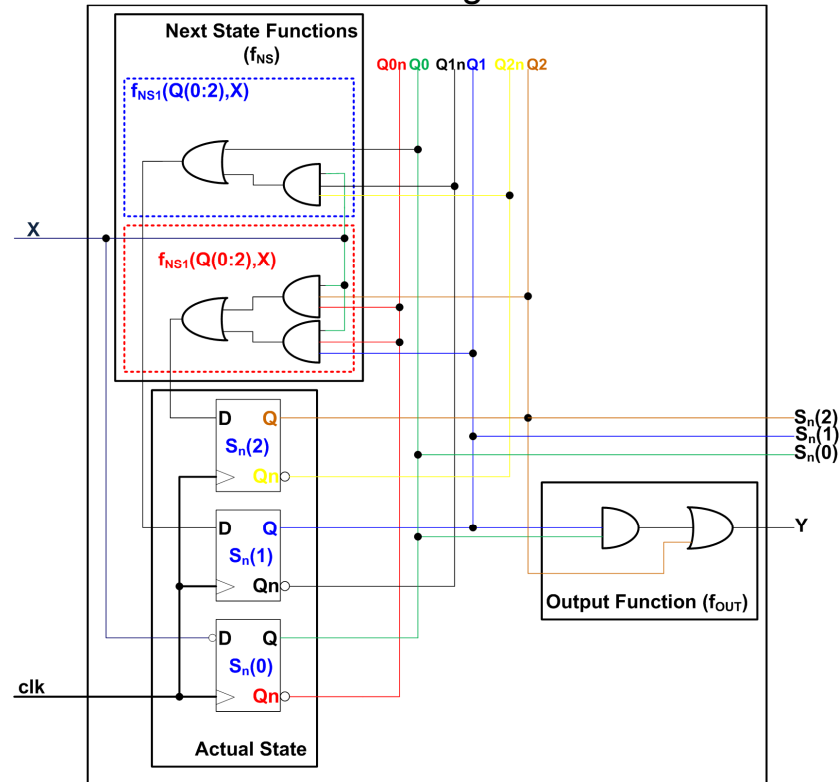
### Exercise 1: Moore FSM Digital Circuit



**Actual State:**

$$S_n(i) = Q(i) \\ (i=0,1,2)$$

**Next State:**

$$S_{n+1}(i) = D(i)$$

**Next-State Functions:**

$$D(i) = f_{NSi}(Q(0:2), X)$$

$$\begin{aligned} D(2) &= Q(1) \cdot \overline{Q(0)} \cdot X + Q(2) \cdot \overline{Q(0)} \cdot \overline{X} \\ D(1) &= Q(0) + \overline{Q(2)} \cdot \overline{Q(1)} \cdot X \\ D(0) &= \overline{X} \end{aligned}$$

Output Function ( $f_{OUT}(S_n)$ ):

$$Y = Q(2) + Q(1) \cdot Q(0)$$

# Finite-State-Machines

## Outline

- Introduction
- Mealy and Moore FSM
- State Diagram
- State Table
- Sequential Synchronous FSM Circuitual Synthesis
- Exercise 1
- Exercise 2
- Exercise 3